

# VE370 RC (Midterm)


## Pipeline & Data hazards

Li Shi


2020.10.17

# Key concept 1: 3 types of microarchitecture


- Single cycle

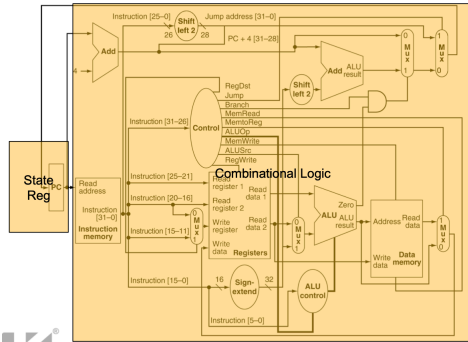

- Multi cycle

 


- Pipeline

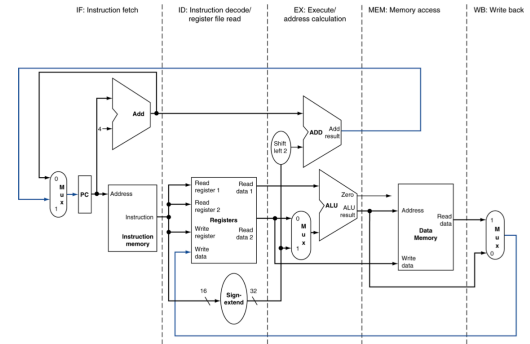


Microarchitecture	CPI	cycle time
Single-cycle unpipelined	1	long
Pipelined	1	short
Multi-cycle, unpipelined control	>1	short
 
# Class exercise 1: Signals in pipelined CPU


- We have 5 instructions in the pipeline.
- Currently the first **lw** instruction is at WB stage.
- Find the values on the following wires.
- (See next slide)



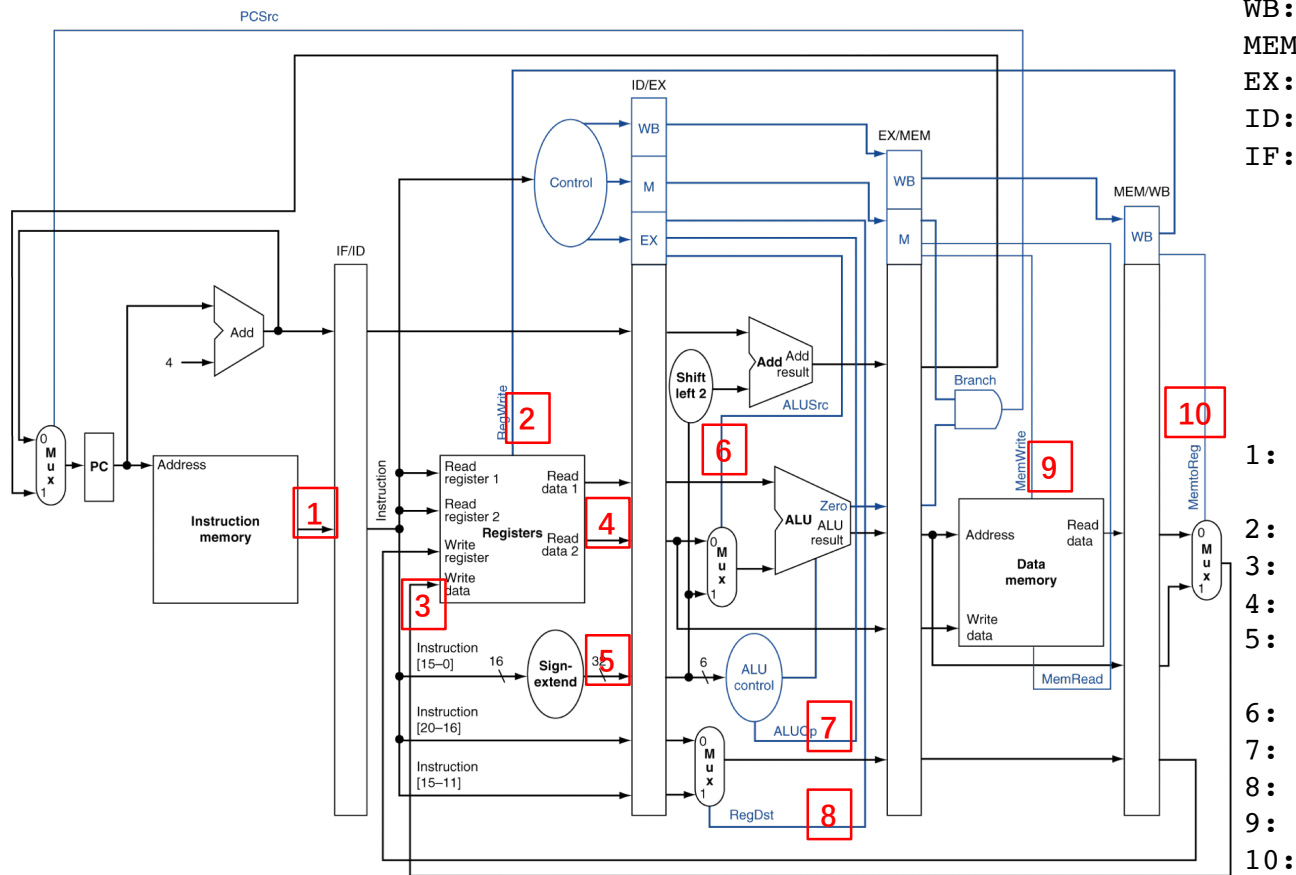

WB: lw \$t0, 20(\$t1)  
 MEM: sub \$t1, \$t2, \$t3  
 EX: add \$t2, \$t3, \$t4  
 ID: lw \$t3, 24(\$t1)  
 IF: add \$t4, \$t5, \$t6

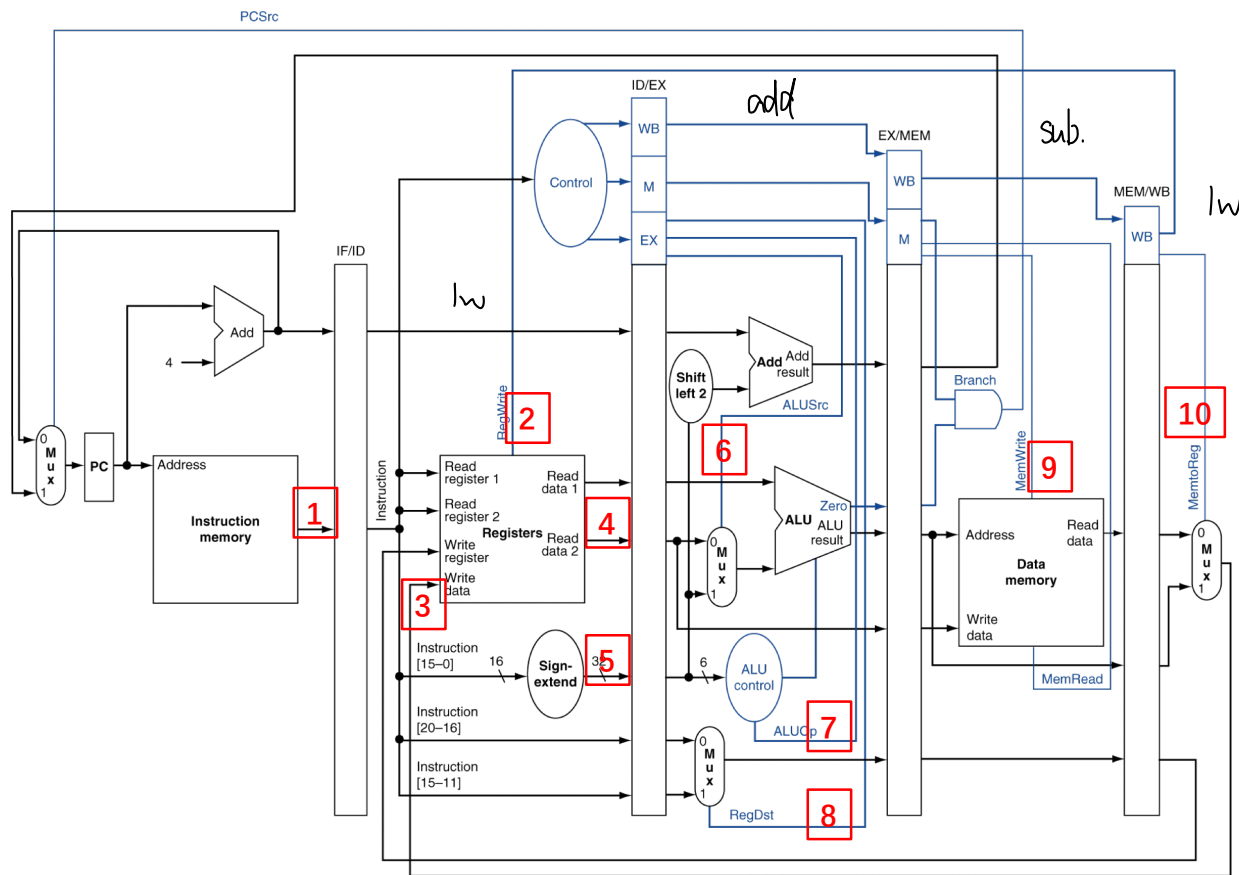1:  
 2:  
 3:  
 4:  
 5:  
 6:  
 7:  
 8:  
 9:  
 10:



WB: lw \$10, 20(\$1)  
 MEM: sub \$11, \$2, \$3  
 EX: add \$12, \$3, \$4  
 ID: lw \$13, 24(\$1)  
 IF: add \$14, \$5, \$6

1: 000000|00101|00110  
 01110|00000|100000  
 2: 1  
 3: ~~0~~ Mem[Reg[\$1]+20]  
 4: ~~0~~ Reg[\$0]  
 5: 0000000000000000  
 (24) 00000000000011000  
 6: 0  
 7: 10  
 8: 1  
 9: 0  
 10: 0

# Key concept 2: 3 types of hazards

- Structural hazards
  - `lw $1, 0($2)`      and      `lw $3, 0($4)`
  - Execute 2 instructions at the same time (so-called superscalar processor), but there is only one read/write port in data memory
  - Simple 5-stage MIPS pipeline has no structural hazards
- Data hazards
  - `add $1, $2, $3`
  - `add $4, $1, $5`
- Control hazards (not covered so far)
  - `add $1, $2, $3`
  - `beq $4, $5, ...`
  - `add $6, $7, $8`

# Key concept 3: Data hazard


- Data hazards occur when one instruction depends on a data value produced by a preceding instruction still in the pipeline
- Approaches to resolving data hazards
  - **Schedule:** Programmer explicitly avoids scheduling instructions that would create data hazards
  - **Stall:** Hardware includes control logic that freezes earlier stages until preceding instruction has finished producing data value
  - **Bypass:** Hardware datapath allows values to be sent to an earlier stage before preceding instruction has left the pipeline



# Key concept 3: Data hazard

- Two kinds of data hazard
  - Solvable by Bypassing or Forwarding Unit
  - Unsolvable, and insert nops
- (We can also avoid hazards and stalls by arranging the code when compiling)

nop 是 forwards 无法解决的.

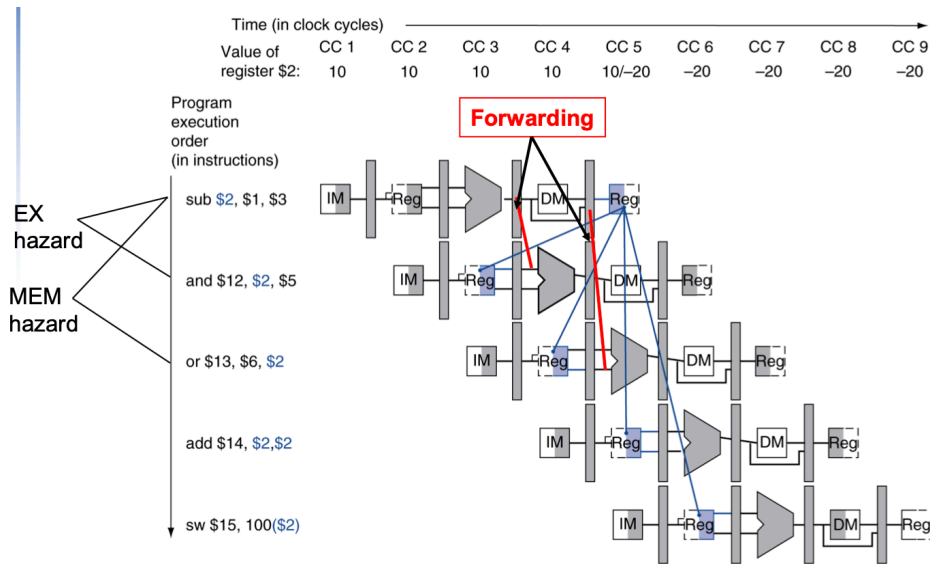



# Key concept 4: Forwarding unit

- 2 important formulas (No need to memorize. Try to understand!)


EX hazard     1 & 2 hazard

- if (EX/MEM.RegWrite and (EX/MEM.RegisterRd  $\neq$  0) and (EX/MEM.RegisterRd == ID/EX.RegisterRs))

**MUX select signal ForwardA = 10**

- if (EX/MEM.RegWrite and (EX/MEM.RegisterRd  $\neq$  0) and (EX/MEM.RegisterRd == ID/EX.RegisterRt))

**MUX select signal ForwardB = 10**

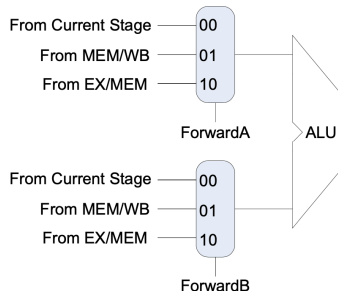

MEM hazard (not EX hazard)     1 & 3 hazard

- if (MEM/WB.RegWrite and (MEM/WB.RegisterRd  $\neq$  0) and (MEM/WB.RegisterRd = ID/EX.RegisterRs) and not (EX/MEM.RegWrite and (EX/MEM.RegisterRd  $\neq$  0) and (EX/MEM.RegisterRd = ID/EX.RegisterRs)))

ForwardA = 01

- if (MEM/WB.RegWrite and (MEM/WB.RegisterRd  $\neq$  0) and (MEM/WB.RegisterRd = ID/EX.RegisterRt) and not (EX/MEM.RegWrite and (EX/MEM.RegisterRd  $\neq$  0) and (EX/MEM.RegisterRd = ID/EX.RegisterRt)))

ForwardB = 01



## Class exercise 2: Signals in forwarding unit

- We have 5 instructions in the pipeline.
- Currently the first **add** instruction is at WB stage.
- Find the values on the following wires.
- (See next slide)

```
WB:  add $1, $1, $2
MEM: add $1, $1, $3
EX:  add $1, $1, $4
ID:  nop
IF:  nop
```


WB: add \$1, \$1, \$2  
 MEM: add \$1, \$1, \$3  
 EX: add \$1, \$1, \$4  
 ID: nop  
 IF: nop

choose latest value

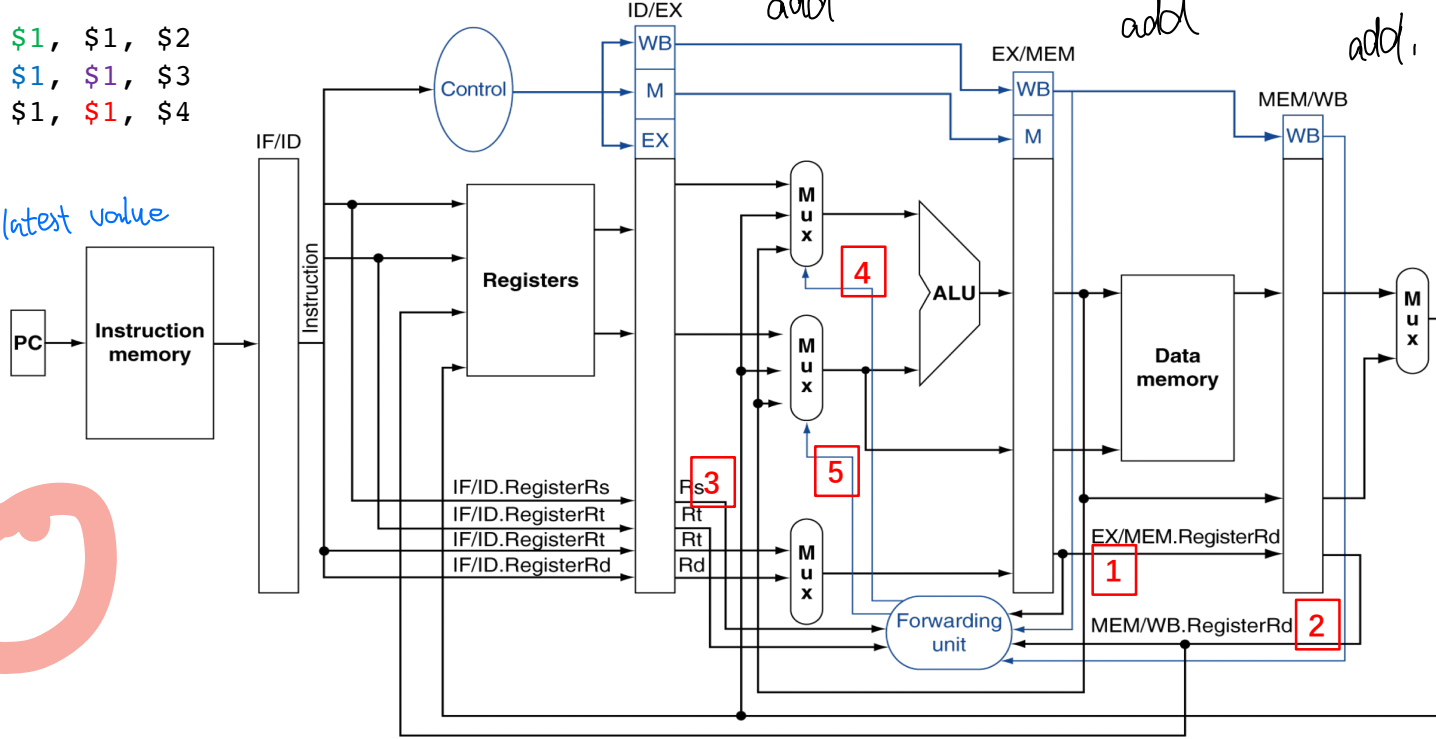 

EX/MEM.RegWrite:	1:	)	4:	10
MEM/WB.RegWrite:	2:		5:	00.
	3:	)		

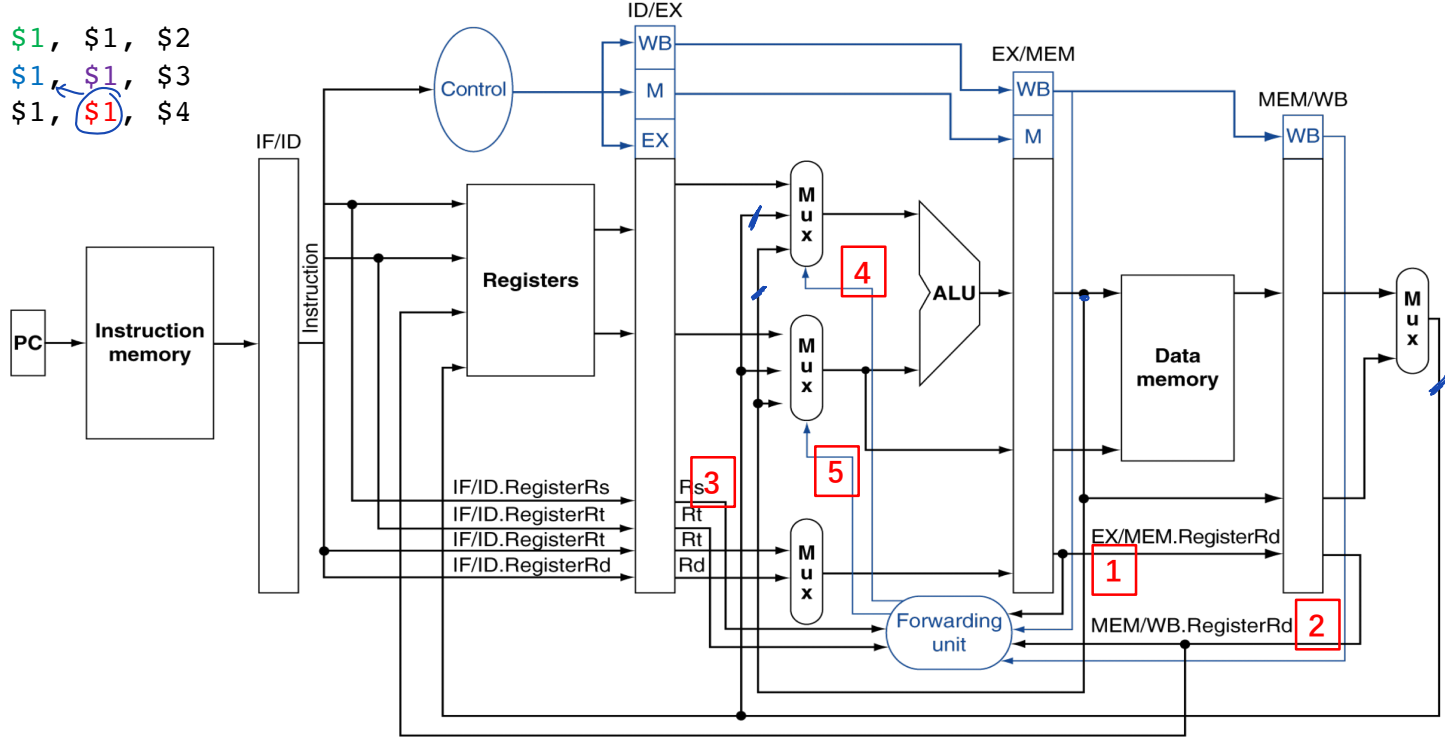WB: add \$1, \$1, \$2  
 MEM: add \$1, \$1, \$3  
 EX: add \$1, \$1, \$4  
 ID: nop  
 IF: nop



EX/MEM.RegWrite: 1  
 MEM/WB.RegWrite: 1

1: 00001  
 2: 00001  
 3: 00001  
 4: 01 (From MEM/WB)  
 5: 00

# Notes

- No calculator. No cheating paper.
- Necessary information will be given in the exam.
- If necessary, you could read the textbook by yourself.
  - *Computer Organization and Design: The Hardware/Software Interface*